

Physics Worksheet: Capacitor Charge & Discharge

Square Signal Excitation (LFG) – MCQ Version

Name: _____

Date: _____

Grade 12

Technical Context: Circuit Parameters

An electrical circuit is set up containing a Low-Frequency Generator (LFG) delivering a square wave voltage u_G , a resistor of resistance R , and a capacitor of capacitance C in series.

The LFG operates with a period T . During the first half-period ($0 \leq t \leq T/2$), the generator delivers a constant voltage E (Charging Phase). During the second half-period ($T/2 \leq t \leq T$), the voltage drops to 0 (Discharging Phase). The time constant of the circuit is $\tau = RC$. The positive direction of current i is chosen to be the direction of the charging current.


Multiple Choice Questions

Circle the single best answer for each question.

- Which equation correctly represents the law of addition of voltages for this series circuit at any instant t ?
 - $u_G = u_C - u_R$
 - $u_C = u_G + u_R$
 - $u_G = u_C + u_R$
 - $u_R = u_G + u_C$
- During the charging phase ($0 \leq t \leq T/2$), the generator voltage u_G is:
 - Steadily increasing from 0 to E .
 - Constant and equal to E .
 - Constant and equal to 0.
 - Decreasing from E to 0.
- How does the voltage across the resistor, u_R , behave during the charging phase?
 - It remains constant at E .
 - It increases from 0 to E .
 - It decreases from E towards 0.
 - It remains constant at 0.
- The relationship between the instantaneous current i and the voltage across the capacitor u_C is given by:
 - $i = \frac{1}{C} \frac{du_C}{dt}$
 - $i = C \cdot u_C$
 - $i = C \frac{du_C}{dt}$
 - $i = R \cdot C \frac{du_C}{dt}$
- During the discharging phase ($T/2 \leq t \leq T$), what is the relationship between u_R and u_C ?

- A. $u_R = u_C$
- B. $u_R = -u_C$


- A. $u_R = u_C$
- B. $u_R = -u_C$

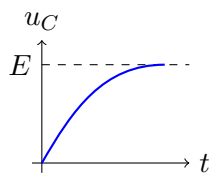


-

- A. Finding the abscissa where the voltage reaches exactly half of its maximum value ($E/2$).
- B. Finding the abscissa of the intersection point between the tangent at $t = 0$ and the horizontal asymptote $u_C = E$.
- C. Finding the abscissa where the tangent at $t = 0$ intersects the horizontal time axis.
- D. Finding the time it takes for the capacitor to reach its maximum voltage E .

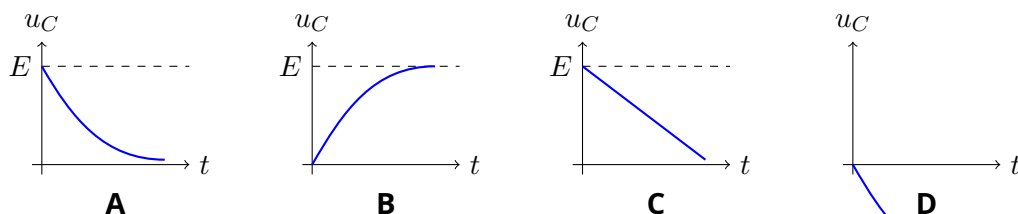13. Which of the following graphs best represents the evolution of the capacitor voltage $u_C(t)$ during the **discharging** phase ($T/2 \leq t \leq T$)?



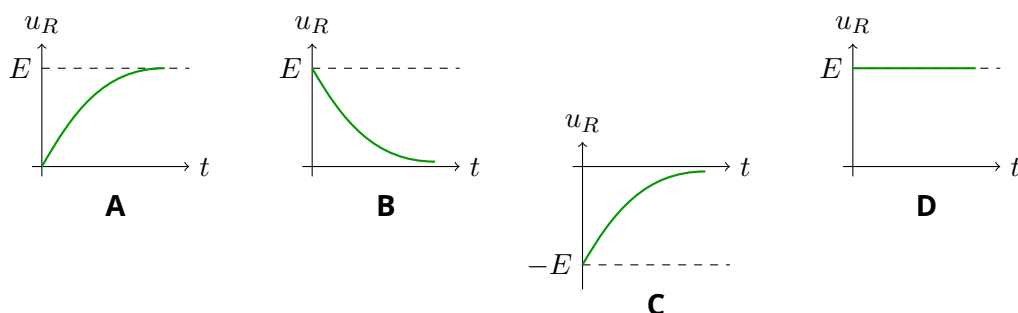14. Which of the following graphs best represents the voltage across the resistor $u_R(t)$ during the **charging** phase ($0 \leq t \leq T/2$)?



15. Based on the relations between $u_R(t)$ and $i(t)$, which of the following accurately describes the evolution of the current $i(t)$ during the **discharging** phase?

- A. It starts at a maximum positive value $\frac{E}{R}$ and decays exponentially to zero.
- B. It is a constant negative value $-\frac{E}{R}$.
- C. It starts at zero and decreases linearly to $-\frac{E}{R}$.
- D. It starts at a maximum negative value $-\frac{E}{R}$ and approaches zero exponentially.

16. (Bonus) When using an oscilloscope with a common ground (Mass) to visualize u_C on Channel Y_1 and u_R on Channel Y_2 simultaneously (as shown in standard circuit diagrams), what must be done to accurately display u_R ?

- A. Add Channel 1 and Channel 2 together using the "MATH" function.
- B. Press the "INVERT" (or reverse) button on Channel 2 because it measures $-u_R$.
- C. Press the "INVERT" button on Channel 1 because it measures $-u_C$.
- D. Change the time-base of the oscilloscope to clearly separate the signals.